

CS231 Digital Logic Design

Week #04

- Express the following numbers in decimal (**Show Your Steps**)
 - $(10110.0101)_2$
22.3125
 - $(16.5)_{16}$
22.3125
 - $(26.24)_8$
22.3125
 - $(DADA.B)_{16}$
56026.6875
 - $(1010.1101)_2$
10.8125
- Perform subtraction on the given unsigned binary numbers using the 2's complement of the subtrahend. Where the result should be negative, find its 2's complement and affix a minus sign.
 - $10011 - 10010 = 00001$
 - $100010 - 100110 = -(000100)$
 - $1001 - 110101 = -(101100)$
 - $101000 - 10101 = 10011$
- Simplify the following Boolean expressions to a minimum
 - $xy + xy' = x$
 - $(x + y)(x + y') = x$
 - $xyz + x'y + xyz' = y$
 - $(A + B)(A' + B') = 0$
 - $(a + b + c')(a'b' + c) = ac + bc + c'a'b'$
 - $a'bc + abc' + abc + a'bc' = b$




CS231 Digital Logic Design

Week #05


1. Draw the logic diagrams of the following circuits using CircuitVerse and establish their truth tables.

a)

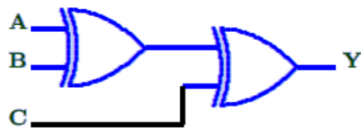

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

b)

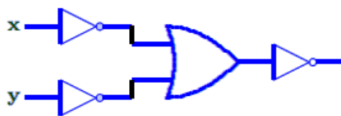


X	Y	F
0	0	0
1	0	0
0	1	0
1	1	1



CS231 Digital Logic Design

c)

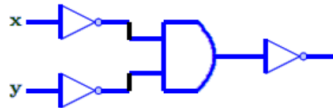

X	Y	F
0	0	0
1	0	1
0	1	1
1	1	1



CS231 Digital Logic Design

2. Simplify the following Boolean expressions to a minimum :

a) $(A+B')(AB'+C)C = CA + CB'$

b) $(A+B')C+(AB'+C).C = C$

c) $((AB)'+(CD)')' = ABCD$


3. Use the Karnaugh table to simplify the following logic equation:

$$X = ABC'D' + AB'CD + ABCD + ABCD' + A'BC'D + A'BCD$$

Draw its logic diagram circuit using CircuitVerse before and after simplification


$$X = A'BD + ACD + ABD'$$

Original circuit

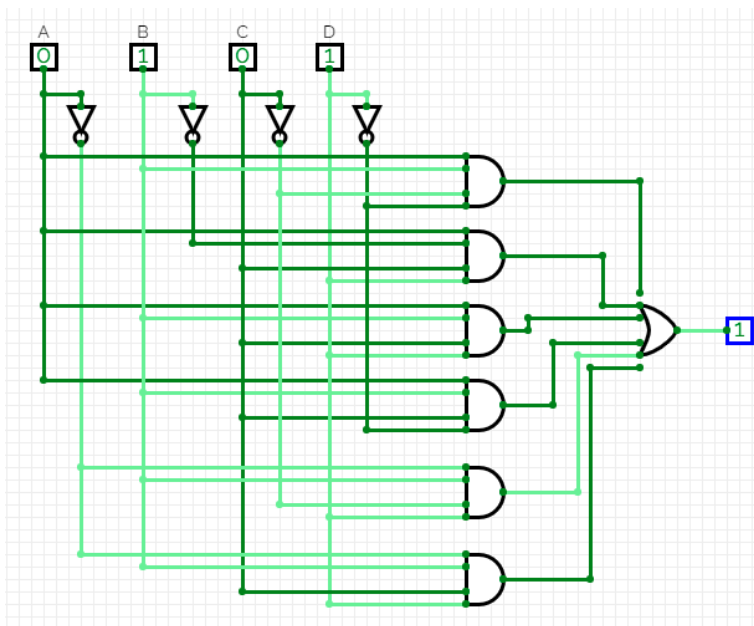

CS231 Digital Logic Design

Simplified circuit

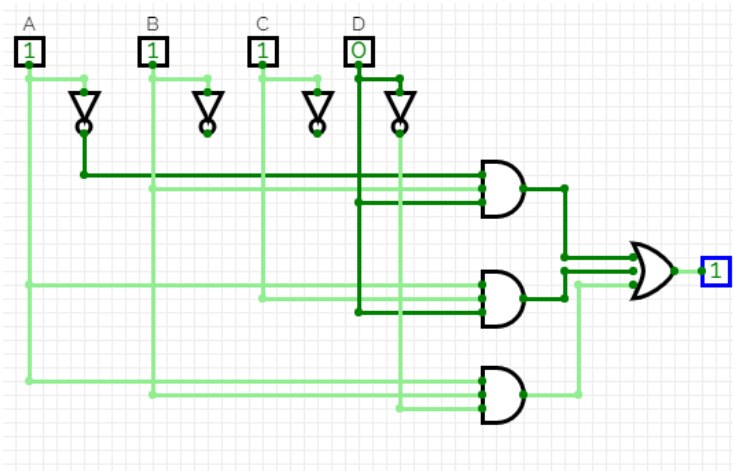

CS231 Digital Logic Design

Week #06 Lab

1. Minimize the following Boolean function using K-map

$$F(A, B, C, D) = \Sigma m(0, 1, 2, 5, 7, 8, 9, 10, 13, 15)$$

$$F(A, B, C, D) = BD + C'D + B'D'$$

2. Minimize the following Boolean function:

$$F(A, B, C) = \Sigma m(0, 1, 6, 7) + \Sigma d(3, 4, 5)$$

$$F = A + B'$$

3. Minimize the following Boolean function and represent it as

a. SOP

b. POS

$$F(A, B, C, D) = \Sigma m(0, 2, 8, 10, 14) + \Sigma d(5, 15)$$

SOP

$$F = A + BC$$



POS

$$F' = A'(B' + C')$$



CS231 Digital Logic Design

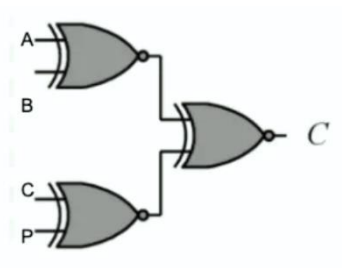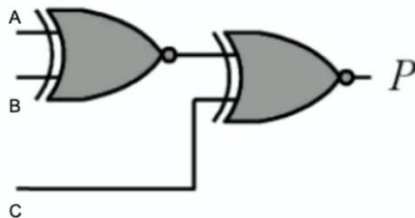4. Derive the circuits for a three-bit parity and four-bit parity generator using an odd parity bit.



CS231 Digital Logic Design

Week #07 Lab


1. Solve the following questions:

- Derive the function from the truth table.
- Simplify the resulted function and draw the logical diagram.
- Finally, convert the diagram to All NAND gates


C	B	A	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$Y = C'A + CB$$

Logical diagram after simplification

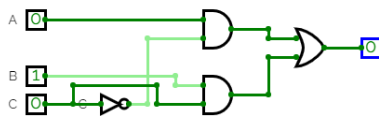


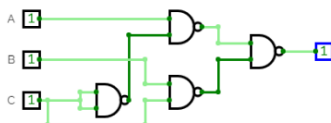Logical diagram after converting all to NAND gates



CS231 Digital Logic Design

2. Consider the combinational circuit

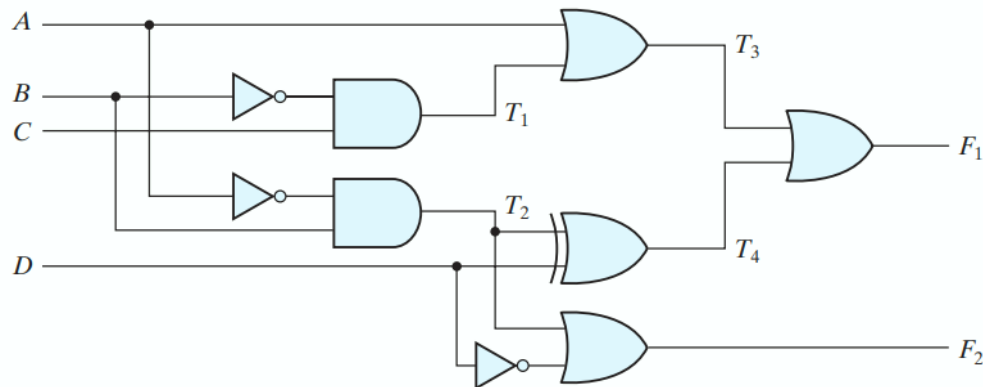

- Derive the Boolean expressions for T1 through T4. Evaluate the outputs F1 and F2 as a function of the four inputs.
- List the truth table with 16 binary combinations of the four input variables. Then list the binary values for T1 through T4 and outputs F1 and F2 in the table.
- Plot the output Boolean functions obtained in part (b) on maps and show that the simplified Boolean expressions are equivalent to the ones obtained in part (a).

$$F1 = A + B'C + BD' + B'D$$

$$F2 = A'B + D'$$



CS231 Digital Logic Design

3. Design a combinational circuit with three inputs and one output. (a)* The output is 1 when the binary value of the inputs is less than 3. The output is 0 otherwise. (b) The output is 1 when the binary value of the inputs is an even number.

You need to follow the design process :

- a) naming variables.
- b) deriving the truth table based on the relationship between the variables.
- c) simplifying the expression of the function by using k-map (or other methods).
- d) drawing the logic diagram.
- e) test with different inputs from the truth table and compare the output you got from the logic diagram

